


Lecture-3

Sequential Circuit Design


Shift Registers

Shift Registers

- Shift register is a digital circuit with two basic functions; data storage and data movement.
- Shift registers contains different arrangements of flip-flops.
- Each flip-flop in a shift register represents one bit of storage capacity.
- The number of flip-flops in a register determines its storage capacity.
- The shift operation of a register allows the movement of data from one stage to another stage or into or out of the register.

 

Concept of storing a 1

 


Concept of storing a 0


Shift Registers

There are four types of shift register based on their movement:


Serial In Serial Out (SISO)

 


Serial In Parallel Out (SIPO)

 

Parallel In Serial Out (PISO)

 


Parallel In Parallel Out (PIPO)

 


Serial In/ Serial Out Shift Registers

 - The serial in/serial out shift registers accepts data serial, that is one bit at a time.
- It produces the stored information in its output also in serial form
- An N-bit flip-flop will take N clock pulses to store N-bit data completely.




Serial In/ Serial Out Shift Registers

 
Four bits (1010) being entered serially into the shift register:




Initial State

 


State after Clock Pulse 1

 

State after Clock Pulse 2

 

State after Clock Pulse 3

 


State after Clock Pulse 4


After CLK4, the 4-bit number is completely stored in register.

Serial In/ Serial Out Shift Registers

 
Four bits (1010) being serially shifted out of the register and replaced by zeros:




State after Clock Pulse 4

 


State after clock pulse 5

 

State after clock pulse 6


 


State after clock pulse 7



 


State after clock pulse 8


Serial In/ Serial Out Shift Registers

  

Serial In/ Parallel Out Shift Registers

   



Parallel In/ Serial Out Shift Registers

 

Shift/ $\overline{LOAD}$ =0, Load line gets activated
Shift/ $\overline{LOAD}$ =1, Shift line gets activated

Parallel In/ Serial Out Shift Registers

  
Show the data-output waveform for a 4-bit register with parallel input data and the clock and SHIFT/LOAD waveform.



Solution:


- On clock pulse 1, the parallel data ($D_0D_1D_2D_3 = 1010$) are loaded into the register making $Q_3 = 0$.
- On clock pulse 2, the 1 from Q_2 is shifted to Q_3 .
- On clock pulse 3, the 0 is shifted on to Q_3 .
- On clock pulse 4, the last bit 1 is shifted on to Q_3 .
- And on clock pulse 5, all data bits have been shifted out, and only 1 remains in the register (assuming D_0 input remains a 1)

 Parallel In/ Parallel Out Shift Registers




Right Left Shift Operation of SISO Shift Registers

For **Right** Shift:

 


For **Left** Shift:

 

Bidirectional Shift Registers



- A bidirectional shift register is one in which data can be shifted either left or right.
- It can be implemented using gating logic.
- This is done with the help of a control input.

Right Shift:

 


Left Shift:

Bidirectional Shift Registers

  

Bidirectional Shift Registers

 Determine the state of the shift register after each clock pulse for the given RIGHT/ $\overline{\text{LEFT}}$ control input waveform. Assume $Q_0 = 1$, $Q_1 = 1$, $Q_2 = 0$, and $Q_3 = 1$ and the serial data input line is LOW.



Shift Register Counters

A shift register counter is basically a shift register with the serial output connected back to the serial input to produce a special sequence. These devices are often classified as counters because they exhibit a specified sequence of states.



Johnson Counters

- In a Johnson counter, the complement of the output of the last flip-flop is connected back to the D input of the first flip-flop.
- This feedback produces a characteristic sequence of states.
- A Johnson counter has $2N$ states, if there are N flip-flops.
- That is a 4-bit sequence has 8 states and a 5-bit sequence has a total of 10 states.

Johnson Counters

Four-bit Johnson sequence.



Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

  

Johnson Counters


Five-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1

  

Ring Counters

 - The ring counter uses one flip-flop for one state in its sequence.
- It has an advantage that decoding gates are not required.
- In case of a 10-bit ring counter, there is an unique output for each decimal digit.



Ring Counters


Ten-bit ring counter sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1



Ring Counters

 If a 10-bit ring counter has an initial state of 1010000000, determine the waveform for each of the Q outputs.



References

1. Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall – Pearson Education.

Thank You